
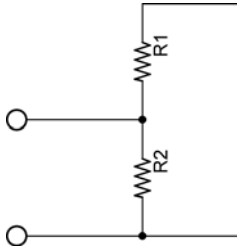


Cornerstone Electronics Technology and Robotics I Week 13 Parallel Circuits Tutorial


- Administration:
 - Prayer
- Electricity and Electronics, **Section 7.1**, Parallel Circuits:
 - A parallel circuit is one that has more than one pathway for the electrons to flow. Unlike series circuit, when you remove a resistor in a parallel circuit, electrons continue to flow.
 - Identifying parallel circuits: Each example below is a circuit with two parallel paths; all of the circuit configurations are electrically equivalent to each other.

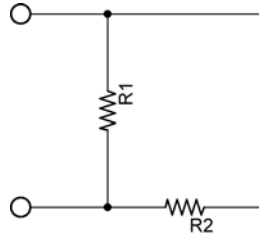


Circuit 1



Circuit 2

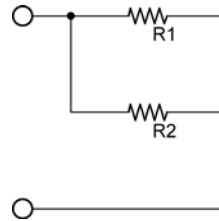

Circuit 3

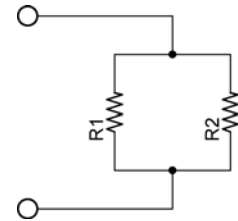

Circuit 4

- Everyday examples of parallel circuits:
 - Electrical outlets in a home See: <http://sol.sci.uop.edu/~jfalward/seriesparallelcircuits/seriesparallelcircuits.html> (House wiring diagram)
 - Lights in a home
 - Electrical car functions, such as the radio, horn, starter, lights, etc.
- **Voltage in a Parallel Circuit:**
 - If components are connected in parallel to the source, the voltage drop across each component is the same as the source voltage.
 - Mathematically:

$$V_T = V_1 = V_2 = V_3 = \dots V_N$$

Where:

V_T = Total voltage applied to the series circuit

V_1 = Voltage drop across R_1

V_2 = Voltage drop across R_2

V_3 = Voltage drop across R_3

V_N = Voltage drop across R_N

N = The number of resistors in the series

- The voltage drop across each component (resistors in this case) is the same. In the two circuits below, the connections in Figure 1 and Figure 2 are electrically equivalent.

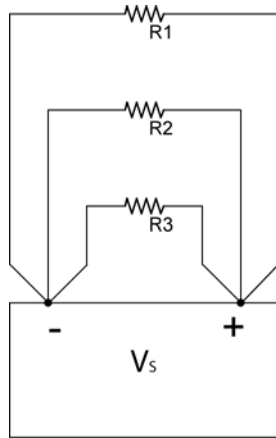


Figure 1

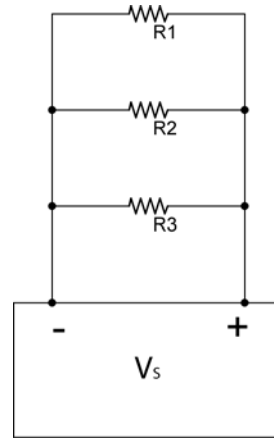


Figure 2

- Perform Parallel Circuits Lab 1 – Voltage Drop in a Parallel Circuit
- **Current in a Parallel Circuit:**
 - Kirchhoff's Current Law: The sum of the currents into a junction is equal to the sum of the currents out of that junction.
 - Mathematically:

$$I_{\text{TOTAL in}} = I_{\text{TOTAL out}}$$

Where:

$I_{\text{TOTAL in}}$ = the sum of currents into a junction

$I_{\text{TOTAL out}}$ = the sum of currents out of a junction

For Example:

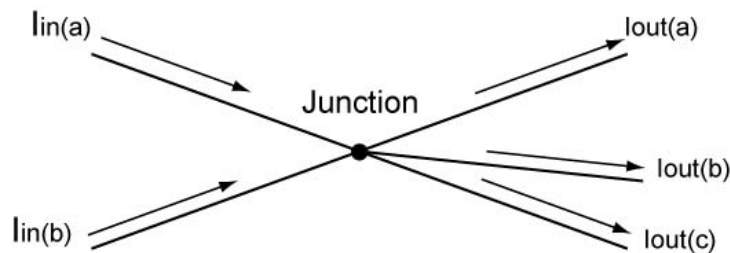


Figure 3

$$I_{\text{in}(a)} + I_{\text{in}(b)} = I_{\text{out}(a)} + I_{\text{out}(b)} + I_{\text{out}(c)}$$

Another way of expressing Kirchhoff's Current Law (see Figure 4):

$$I_T = I_1 + I_2 + I_3 + \dots + I_N$$

Where:

I_T = Total current into a parallel resistor circuit

I_1 = Current through R_1

I_2 = Current through R_2

I_3 = Current through R_3

I_N = Current through R_N


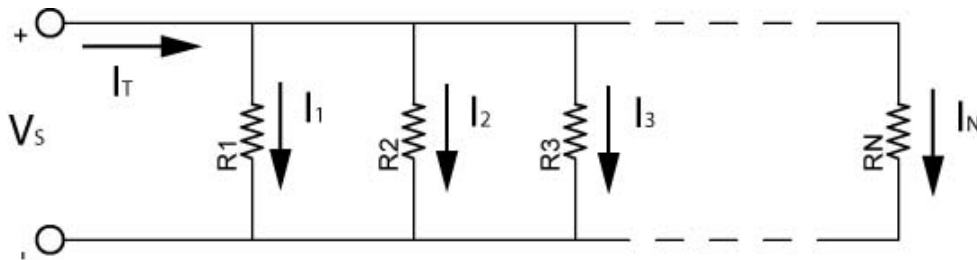


Figure 4

- See applets:
 - <http://www.falstad.com/circuit/e-ohms.html>
 - http://media.pearsoncmg.com/bc/aw_young_physics_11/pt2a/Media/DCCircuits/1202DCParallel/Main.html (#3, junction law)
- Parallel circuits act as current dividers. See the two examples below.

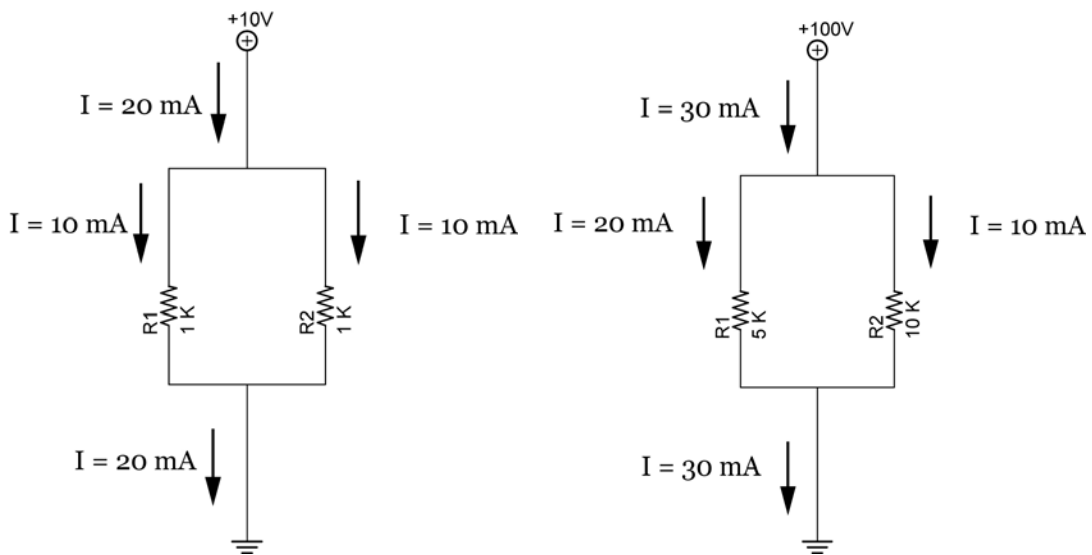

Example 1

Example 2

- Perform Parallel Circuits Lab 2 – Kirchhoff's Current Law

○ **Resistance in Parallel Circuits:**

- When resistors are connected in parallel circuits, the total resistance is always less than the value of the smallest resistor.

- **Reciprocal Rule:**

- The reciprocal of a number is equal to 1 divided by that number, e.g., the reciprocal of 4 is 1/4, and the reciprocal of 87 is 1/87.
- The total resistance of a parallel circuit is:

$$1/R_T = 1/R_1 + 1/R_2 + 1/R_3 + \dots + 1/R_N$$

Where R_T is the total resistance and

N is the total number of resistors in parallel.

- **Proof:** Since $I_T = I_1 + I_2 + I_3 + \dots + I_N$:


And $I_T = V_S/R_T$ and $I_1 = V_S/R_1$, $I_2 = V_S/R_2$, etc., then:

$$V_S/R_T = V_S/R_1 + V_S/R_2 + V_S/R_3 + \dots + V_S/R_N$$

Now factor out V_S by dividing both sides of the equation by V_S and you arrive at:

$$1/R_T = 1/R_1 + 1/R_2 + 1/R_3 + \dots + 1/R_N$$

- For example, find the total resistance in Circuit 5:

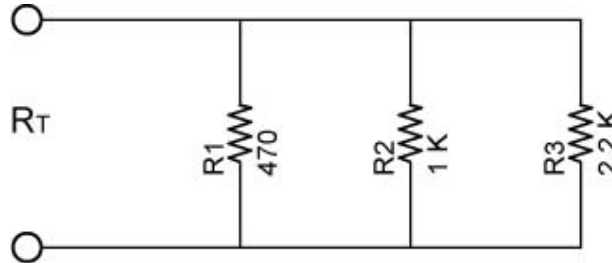

Circuit 5

$$1/R_T = 1/R_1 + 1/R_2 + 1/R_3$$

$$1/R_T = 1/470 + 1/1000 + 1/2200$$

$$1/R_T = 0.0021 + 0.001 + 0.0004$$

$$1/R_T = 0.0035$$

$$R_T = 1/0.0035$$

$$R_T = 286 \Omega$$

- **Special Case 1:** Two resistor parallel circuit: If $1/R_T = 1/R_1 + 1/R_2$, then

$$R_T = R_1 R_2 / R_1 + R_2$$


- Special Case 2: Resistors of equal value:

$$R_T = R/N$$

Where:

R = the value of each resistor (all being the same)
 N = the number of resistors

For Example:

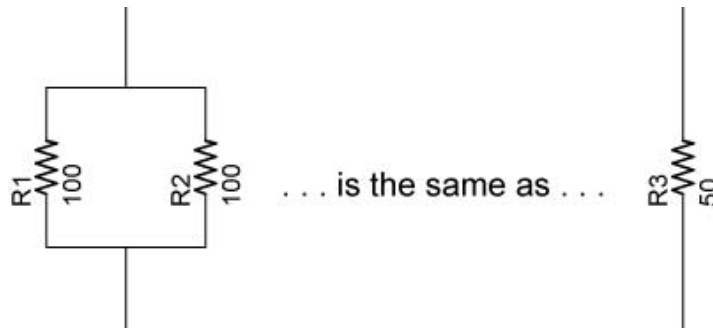

$$R_T = R/N$$

$$R_T = 100/2$$

$$R_T = 50 \Omega$$

How many 1 K resistors in parallel would you need to create a total resistance of 1 ohm?

- In a parallel circuit, a resistor that is much smaller than the other resistors dominates.
 - Applet: <http://www.lon-capa.org/~mmp/kap20/RR506a.htm>
 - Perform Parallel Circuits Lab 3 – Total Resistance in a Parallel Circuit
- **Power in a Parallel Circuit:**
- The total power is equal to the sum of all the power of each resistor in the parallel circuit.

$$P_T = P_1 + P_2 + P_3 + \dots + P_N$$

Where P_T is the total power consumed in the circuit and
 N is the total number of resistors in parallel.

- Power is also equal to the source voltage times the total current.

$$P_T = V_T \times I_T$$

Where P_T is the total power consumed in the circuit,
 V_T is the source voltage, and
 I_T is the total current

- Electricity and Electronics, **Section 7.2**, Applications and Troubleshooting Parallel Circuits:

- Solving for Resistance, Voltage, and Current in a Parallel Resistor Circuits:

- Four equations are used to solve parallel resistor circuits. They are:

$$1/R_T = 1/R_1 + 1/R_2 + 1/R_3 + \dots + 1/R_N$$

$$V_T = V_1 = V_2 = V_3 = \dots = V_N$$

$$I_T = I_1 + I_2 + I_3 + \dots + I_N$$

$$V = I \times R$$

$V = I \times R$ can be applied to the total circuit ($V_T = I_T \times R_T$) and to individual resistors ($V_1 = I_1 \times R_1$).

- A table will be used to help solve our circuits. To begin, a table as shown in Table 1 corresponds to the circuit in Figure 5:

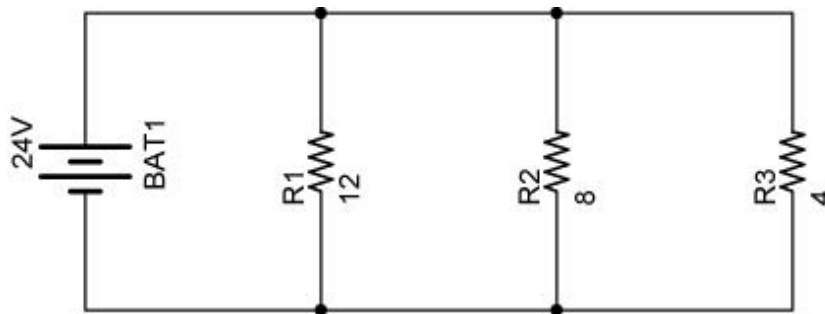


Figure 5

	Resistance	Voltage	Current
R1	R1 = 12 Ω		
R2	R2 = 8 Ω		
R3	R3 = 4 Ω		
Total		V _T = 24 V	

Table 1

- Table 2 lists all of the unknowns that will be solved.

	Resistance	Voltage	Current
R1	R1 = 12 Ω	V1	I1
R2	R2 = 8 Ω	V2	I2
R3	R3 = 4 Ω	V3	I3
Total	R _T	V _T = 24 V	I _T

Table 2

- Step 1: Find V_1 , V_2 , and V_3 .

$$V_T = V_1 = V_2 = V_3 = 24 \text{ V}$$

See Table 3:

	Resistance	Voltage	Current
R1	$R1 = 12 \Omega$	$V1 = 24 \text{ V}$	I_1
R2	$R2 = 8 \Omega$	$V2 = 24 \text{ V}$	I_2
R3	$R3 = 4 \Omega$	$V3 = 24 \text{ V}$	I_3
Total	R_T	$V_T = 24 \text{ V}$	I_T

Table 3

- Step 2: Find I_1 , I_2 , and I_3 .

$$V_1 = I_1 \times R_1, \text{ therefore,}$$

$$I_1 = V_1 / R_1$$

$$I_1 = 24 \text{ V} / 12 \Omega$$

$$I_1 = 2 \text{ A}$$

$$I_2 = V_2 / R_2$$

$$I_2 = 24 \text{ V} / 8 \Omega$$

$$I_2 = 3 \text{ A}$$

$$I_3 = V_3 / R_3$$

$$I_3 = 24 \text{ V} / 4 \Omega$$

$$I_3 = 6 \text{ A}$$

See Table 4:

	Resistance	Voltage	Current
R1	$R1 = 12 \Omega$	$V1 = 24 \text{ V}$	$I1 = 2 \text{ A}$
R2	$R2 = 8 \Omega$	$V2 = 24 \text{ V}$	$I2 = 3 \text{ A}$
R3	$R3 = 4 \Omega$	$V3 = 24 \text{ V}$	$I3 = 6 \text{ A}$
Total	R_T	$V_T = 24 \text{ V}$	I_T

Table 4

- Step 3: Find I_T .

$$I_T = I_1 + I_2 + I_3$$

$$I_T = 2 \text{ A} + 3 \text{ A} + 6 \text{ A}$$

$$I_T = 11 \text{ A}$$

See Table 5:

	Resistance	Voltage	Current
R1	$R1 = 12 \Omega$	$V1 = 24 \text{ V}$	$I1 = 2 \text{ A}$
R2	$R2 = 8 \Omega$	$V2 = 24 \text{ V}$	$I2 = 3 \text{ A}$
R3	$R3 = 4 \Omega$	$V3 = 24 \text{ V}$	$I3 = 6 \text{ A}$
Total	R_T	$V_T = 24 \text{ V}$	$I_T = 11 \text{ A}$

Table 5

- Step 5: Find R_T .

$$1/R_T = 1/R_1 + 1/R_2 + 1/R_3$$

$$1/R_T = 1/12 + 1/8 + 1/4$$

$$1/R_T = 0.083 + 0.125 + 0.25$$

$$1/R_T = 0.458$$

$$R_T = 1/0.458$$

$$R_T = 2.18 \Omega$$

Or an alternate way:

$$V_T = I_T \times R_T, \text{ therefore,}$$

$$R_T = V_T / I_T$$

$$R_T = 24 \text{ V} / 11 \text{ A}$$

$$R_T = 2.18 \Omega$$

See Table 6:

	Resistance	Voltage	Current
R1	$R1 = 12 \Omega$	$V1 = 24 \text{ V}$	$I1 = 2 \text{ A}$
R2	$R2 = 8 \Omega$	$V2 = 24 \text{ V}$	$I2 = 3 \text{ A}$
R3	$R3 = 4 \Omega$	$V3 = 24 \text{ V}$	$I3 = 6 \text{ A}$
Total	$R_T = 2.18 \Omega$	$V_T = 24 \text{ V}$	$I_T = 11 \text{ A}$

Table 6

- Since all of the resistances, voltages, and currents are solved in the present problem, the power can now be calculated.

- Solving for Power in a Parallel Resistor Circuits:
 - Two equations are used to solve for power in a parallel resistor circuit. They are:

$$P_T = P_1 + P_2 + P_3 + \dots + P_N$$

$$P = V \times I$$

$P = V \times I$ can be applied to the total circuit ($P_T = V_T \times I_T$) and to individual resistors ($P_1 = V_1 \times I_1$).

- A column for power will be added to the table already used to solve our circuit. See Table 7.

	Resistance	Voltage	Current	Power
R1	R1 = 12 Ω	V1 = 24 V	I1 = 2 A	P1
R2	R2 = 8 Ω	V2 = 24 V	I2 = 3 A	P2
R3	R3 = 4 Ω	V3 = 24 V	I3 = 6 A	P3
Total	R _T = 2.18 Ω	V _T = 24 V	I _T = 11 A	P _T

Table 7

- Step 5: Solve for P_1 , P_2 , P_3 , and P_T .

$$P_1 = V_1 \times I_1$$

$$P_1 = 24 \text{ V} \times 2 \text{ A}$$

$$P_1 = 48 \text{ W}$$

$$P_2 = V_2 \times I_2$$

$$P_2 = 24 \text{ V} \times 3 \text{ A}$$

$$P_2 = 72 \text{ W}$$

$$P_3 = V_3 \times I_3$$

$$P_3 = 24 \text{ V} \times 6 \text{ A}$$

$$P_3 = 144 \text{ W}$$

$$P_T = P_1 + P_2 + P_3$$

$$P_T = 48 \text{ W} + 72 \text{ W} + 144 \text{ W}$$


$$P_T = 264 \text{ W}$$

See Table 8:

	Resistance	Voltage	Current	Power
R1	R1 = 12 Ω	V1 = 24 V	I1 = 2 A	P1 = 48 W
R2	R2 = 8 Ω	V2 = 24 V	I2 = 3 A	P2 = 72 W
R3	R3 = 4 Ω	V3 = 24 V	I3 = 6 A	P3 = 144 W
Total	R _T = 2.18 Ω	V _T = 24 V	I _T = 11 A	P _T = 264 W

Table 8

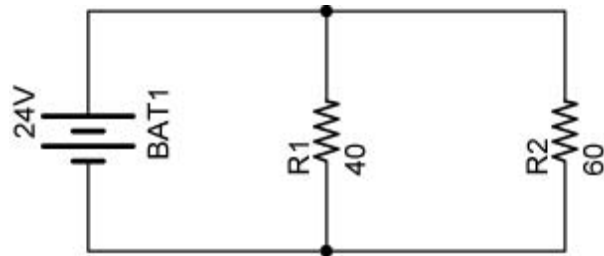- Example Problem 1:
 - Solve for all of the unknowns in the following circuit. Fill in each unknown in the table below the circuit.



	Resistance	Voltage	Current	Power
R ₁	R1 = 40 Ω			
R ₂	R2 = 60 Ω			
Total		V _T = 24 V		

- Remember:


$$1/R_T = 1/R_1 + 1/R_2 + 1/R_3 + \dots + 1/R_N$$

$$V_T = V_1 = V_2 = V_3 = \dots = V_N$$

$$I_T = I_1 + I_2 + I_3 + \dots + I_N$$

$$V = I \times R$$

○ Example Problem 2:

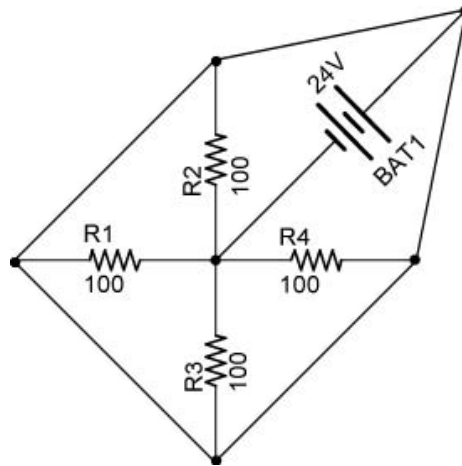

	Resistance	Voltage	Current	Power
R ₁	R1 = 100 Ω			
R ₂	R2 = 100 Ω			
R ₃	R3 = 100 Ω			
R ₄	R4 = 100 Ω			
Total		V _T = 24 V		

○ Equations:


$$1/R_T = 1/R_1 + 1/R_2 + 1/R_3 + \dots + 1/R_N$$

$$V_T = V_1 = V_2 = V_3 = \dots = V_N$$

$$I_T = I_1 + I_2 + I_3 + \dots + I_N$$


$$V = I \times R$$

○ Example Problem 3:

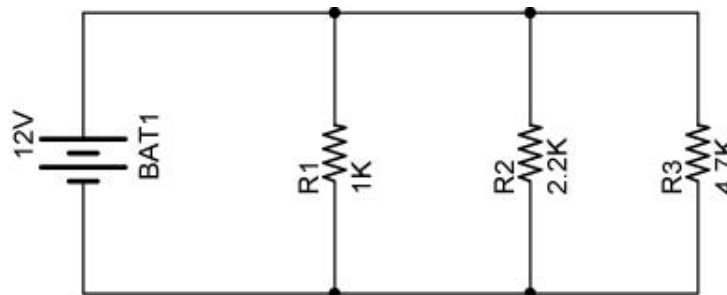


	Resistance	Voltage	Current	Power
R ₁	R1 = 1K Ω			
R ₂	R2 = 2.2K Ω			
R ₃	R3 = 4.7K Ω			
Total		V _T = 12 V		

- Example Problem 4:

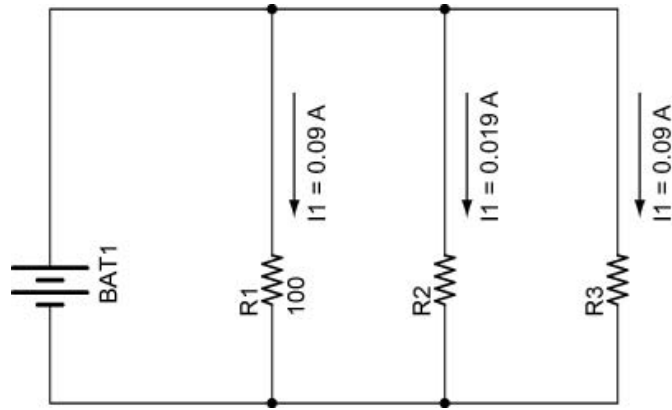

	Resistance	Voltage	Current	Power
R ₁	R1 = 100 Ω		I1 = 0.09 A	
R ₂			I2 = 0.019 A	
R ₃			I3 = 0.09 A	
Total				

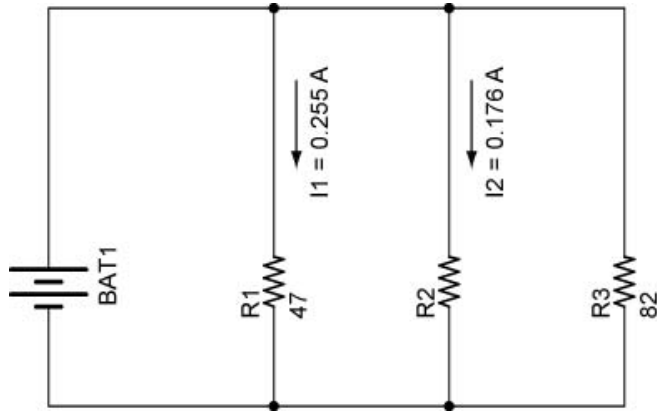- Example Problem 5:
 - Setup the table and solve for the unknowns:



	Resistance	Voltage	Current	Power
R ₁				
R ₂				
R ₃				
Total				

- Table setup:

	Resistance	Voltage	Current	Power
R ₁	R1 = 47 Ω		I1 = 0.255 A	
R ₂			I2 = 0.176 A	
R ₃	R3 = 82 Ω			
Total				

- Solve problems 1, 2, 4, and 7 in Student Activity Sheet 7-2.
- Related Web Sites:
 - http://www.physics247.com/solved_problems/basic_circuits.php
 - <http://www.acs.ryerson.ca/~kantorek/EES512/tutor2.html>
 - <http://people.clarkson.edu/~svoboda/eta/designLab/ParallelRDesign.html>
 - <http://www.glenbrook.k12.il.us/gbssci/phys/Class/circuits/u9l4d.html>
 - http://www.allaboutcircuits.com/vol_1/chpt_5/3.html
- Suggested Home-Study Student Activity Sheets 7.1 and 7.2

- Example Problem Solutions:
 - Example Problem 1:

	Resistance	Voltage	Current	Power
R ₁	R1 = 40 Ω	V1 = 24 V	I1 = 0.6 A	P1 = 14.4 W
R ₂	R2 = 60 Ω	V2 = 24 V	I2 = 0.4 A	P2 = 9.6 W
Total	R _T = 24 Ω	V _T = 24 V	I _T = 1.0 A	P _T = 24.0 W

- Example Problem 2:

	Resistance	Voltage	Current	Power
R ₁	R1 = 100 Ω	V1 = 24 V	I1 = 0.24 A	P1 = 5.76 W
R ₂	R2 = 100 Ω	V2 = 24 V	I2 = 0.24 A	P2 = 5.76 W
R ₃	R3 = 100 Ω	V3 = 24 V	I3 = 0.24 A	P3 = 5.76 W
R ₄	R4 = 100 Ω	V4 = 24 V	I4 = 0.24 A	P4 = 5.76 W
Total	R _T = 25 Ω	V _T = 24 V	I _T = 0.96 A	P _T = 23.04 W

- Example Problem 3:

	Resistance	Voltage	Current	Power
R ₁	R1 = 1K Ω	V1 = 12 V	I1 = 0.012 A	P1 = 0.144 W
R ₂	R2 = 2.2K Ω	V2 = 12 V	I2 = 0.0055 A	P2 = 0.066 W
R ₃	R3 = 4.7K Ω	V3 = 12 V	I3 = 0.0025 A	P3 = 0.03 W
Total	R _T = 600 Ω	V _T = 12 V	I _T = 0.020 A	P _T = 0.24 W

- Example Problem 4:


	Resistance	Voltage	Current	Power
R ₁	R1 = 100 Ω	V1 = 9V	I1 = 0.09 A	P1 = 0.81 W
R ₂	R2 = 484 Ω	V2 = 9 V	I2 = 0.019 A	P2 = 0.171 W
R ₃	R3 = 100 Ω	V3 = 9 V	I3 = 0.09 A	P3 = 0.81 W
Total	R _T = 45 Ω	V _T = 9 V	I _T = 0.20 A	P _T = 1.79 W

- Example Problem 5:

	Resistance	Voltage	Current	Power
R ₁	R1 = 47 Ω	V1 = 12 V	I1 = 0.255 A	P1 = 3.06 W
R ₂	R2 = 68 Ω	V2 = 12 V	I2 = 0.176 A	P2 = 2.11 W
R ₃	R3 = 82 Ω	V3 = 12 V	I3 = 0.146 A	P3 = 1.75 W
Total	R _T = 20.7 Ω	V _T = 12 V	I _T = 0.577 A	P _T = 6.92 W

Electronics Technology and Robotics I Week 13
Parallel Circuits Lab 1 – Voltage Drop in a Parallel Circuit

- **Purpose:** The purpose of this lab is to experimentally verify that the voltage drops across parallel resistors are equal.
- **Apparatus and Materials:**
 - 1 – Solderless Breadboard with 9 V Power Supply
 - 1 – Digital Multimeter
 - 1 – 1 K Ohm Resistor
 - 2 – 2.2 K Ohm Resistors
 - 1 – 4.7 K Ohm Resistor
- **Procedure:**
 - Wire the following circuit
 - Measure and record V_{AE} , V_{BF} , V_{CG} , and V_{DH} .

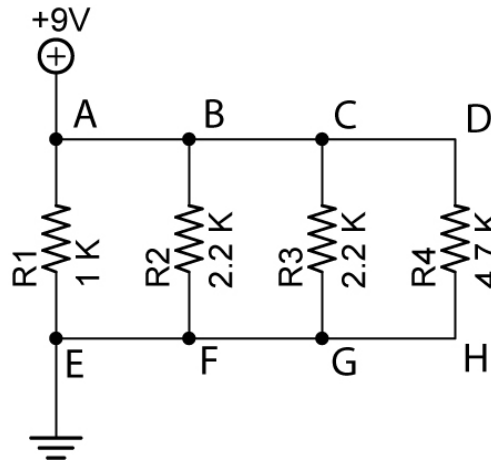


- **Results:**

Points	Voltage Drop
A - E	
B - F	
C - G	
D - H	

- **Conclusions:**
 - How do the voltage drops V_{AE} , V_{BF} , V_{CG} , and V_{DH} relate to each other?

Electronics Technology and Robotics I Week 13 Parallel Circuits Lab 2 – Kirchhoff's Current Law

- **Purpose:** The purpose of this lab is to experimentally verify Kirchhoff's Current Law.
- **Apparatus and Materials:**
 - 1 – Solderless Breadboard with 9 V Power Supply
 - 4 – Digital Multimeters
 - 4 - Switches
 - 2 – 220 Ohm Resistors
 - 1 – 330 Ohm Resistor
 - 1 – 470 Ohm Resistor
- **Procedure:**
 - In the following circuit, simultaneously measure the current at points A, B, C, and D. With all switches closed, see if $I_A = I_B + I_C + I_D$. Record the results. Measure and record the currents of the other combinations in the table using open and closed switches.
 - Verify Kirchhoff's Current Law for each case.

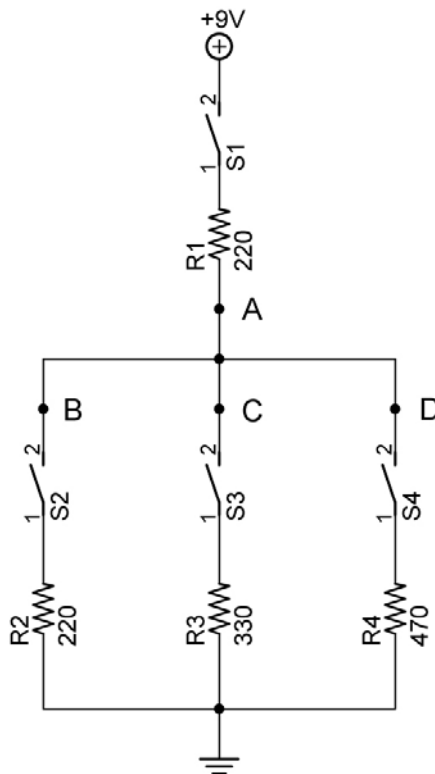

Note how the current through R_1 changes as resistors R_2 , R_3 , and R_4 are added or removed from the circuit.

- **Results:**

Current In	Currents Out			Total of Currents Out
I_A (mA)	I_B (mA)	I_C (mA)	I_D (mA)	Total (mA)
				$I_B + I_C + I_D =$
				$I_B + I_C =$
				$I_B + I_D =$
				$I_C + I_D =$
				$I_B =$
				$I_C =$
				$I_D =$

- **Conclusions:**

- Does the experiment verify Kirchhoff's Current Law? Explain.

Electronics Technology and Robotics I Week 13

Parallel Circuits Lab 3 – Total Resistance in a Parallel Circuit

- **Purpose:** The purpose of this lab is to experimentally verify the reciprocal rule for total resistance of a parallel circuit.


- **Apparatus and Materials:**

- 1 – Solderless Breadboard
- 1 – Digital Multimeter
- 1 – 100 Ohm Resistors
- 1 – 220 Ohm Resistors
- 3 – 1500 Ohm Resistor

- **Procedure:**


- Resistors in Parallel:

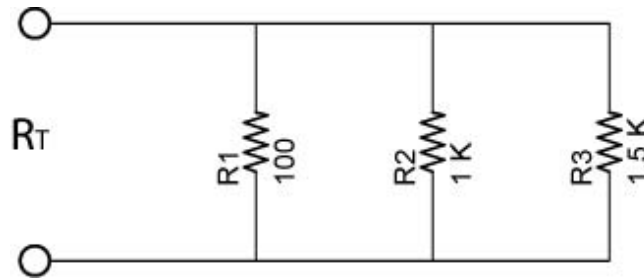- Wire the following circuit below then calculate and measure/record R_T .




- Two Parallel Resistors:

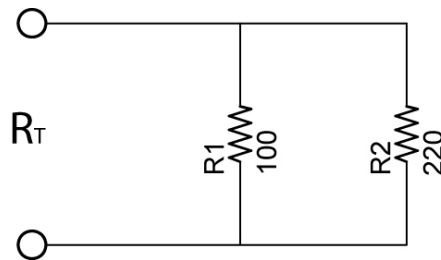- Wire the following circuit below then calculate and measure/record R_T .



- Equal Resistors:

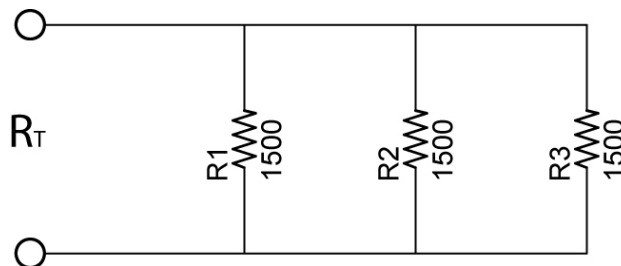- Wire the following circuit below then calculate and measure/record R_T .



- **Results:**

- Resistors in Parallel:

R_T Calculated	R_T Measured

- Two Parallel Resistors:

R_T Calculated	R_T Measured

- Equal Resistors:

R_T Calculated	R_T Measured

- **Conclusions:** In each case, evaluate how well the R_T calculated matched the R_T measured. Explain any discrepancies.

- Resistors in Parallel:

$$1/R_T = 1/R_1 + 1/R_2 + 1/R_3 + \dots + 1/R_N$$

- Two Parallel Resistors:

$$R_T = R_1 R_2 / (R_1 + R_2)$$

- Equal Resistors:

$$R_T = R/N$$